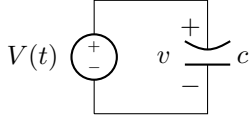



# Lecture 22, Mar 9, 2022
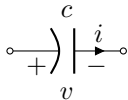
## Capacitors

- A capacitor consists of 2 conducting plates separated by an insulator; when connected to a voltage, charges accumulate on the plates, creating an electric field and storing energy:



- The accumulated charge is proportional to the voltage:  $q(t) = cv(t)$ 
  - \*  $c$  is the *capacitance*, and is determined by the physical characteristics of the capacitor (similar to resistance for a resistor)
  - \* Capacitance has units of Coulombs per volt or farads:  $C/V = F$ 
    - In practice one farad is a very large capacitance; most capacitors are in the order of microfarads or smaller
- Translating this into current:  $i = \frac{dq}{dt} = \frac{d}{dt}cv(t) \implies i(t) = c\frac{dv}{dt}$ 
  - Current passing through a capacitor is proportional to the rate of change of voltage
  - This relation holds if PSC holds; otherwise  $i = -c\frac{dv}{dt}$
- In the other direction:  $\int_{t_1}^{t_2} c\frac{dv}{dt} dt = \int_{t_1}^{t_2} i(t) dt \implies v(t_2) - v(t_1) = \frac{1}{c} \int_{t_1}^{t_2} i(t) dt$ 
  - $v(t) = v(0) + \frac{1}{c} \int_0^t i(\tau) d\tau$
  - To find the voltage of a capacitor at time  $t$ , integrate the current
  - We need both the current function and a known value of  $v(t)$ , unlike with current from voltage where we only need the voltage function
- Properties of capacitors:



1. If the voltage is constant (i.e. DC), then current is always 0, since  $\frac{dv}{dt}$  is 0
    - A capacitor can be modelled as an open circuit in a DC circuit
  2. The voltage of a capacitor cannot change abruptly; a discontinuity in voltage creates an infinite  $\frac{dv}{dt}$  and infinite current
- Find energy of a capacitor:  $W(t_2) - W(t_1) = \int_{t_1}^{t_2} P(t) dt$ 

$$= \int_{t_1}^{t_2} v(t)i(t) dt$$

$$= \int_{t_1}^{t_2} cv(t)\frac{dv}{dt} dt$$

$$= c \int_{t_1}^{t_2} v dv$$

$$= \frac{1}{2}c(v^2(t_2) - v^2(t_1))$$
    - Assuming capacitor is unchanged at  $t = 0$  (i.e.  $v(0) = 0$ ),  $W(t) = \frac{1}{2}cv^2(t)$
    - An ideal capacitor does not dissipate energy; it only stores and delivers energy
  - Although an ideal capacitor stops all DC current, a physical capacitor has some leakage current
  - A real capacitor can be modelled as an ideal capacitor in parallel with a *leakage resistance* of  $R_L$ , typically in the hundreds of megaohms